
# Coffee Bean Roaster

Carlson Jansen Andrew Liu Mirwais Lodin Liam McHugh

# Project Overview and Name ~1 min


- Our project aims for implementing a functional precision temperature control for equipment like a Coffee Bean Roaster, by recycling simple popcorn maker with built in heater, fan, and AC power distribution.
- The project will dive into recreating thermocouple module, AC or DC heat fan dimmer/control board, wall plug AC/DC converter, additional app/GUI control on screen display.
- Major challenges would be precise feedback control of temperature in the chamber, additional serial peripheral interface bus may be required if multiple thermocouple is desired.
- ESP32, K-Type Thermocouple, 16x4 LCD
- Overall circuit designs (filter types, power regulator type, power source, microcontroller used, important sensors, actuators or ICs, data buses used)

## BOM ~30 sec

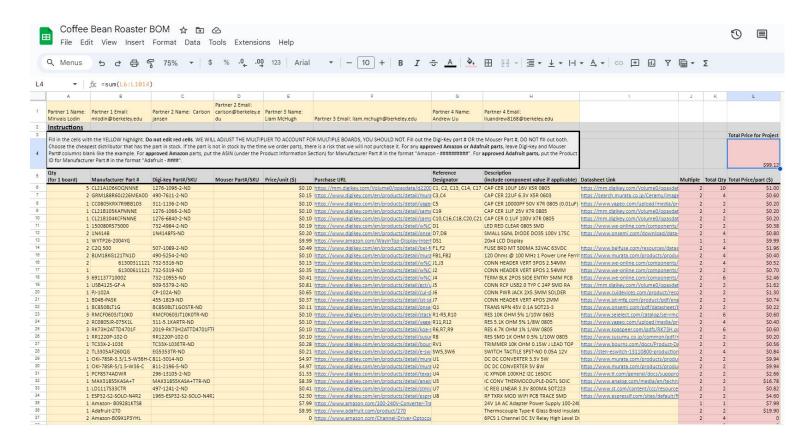

Voltage drop down module: DC-DC Converters

24V to 3.3V 24V to 5V

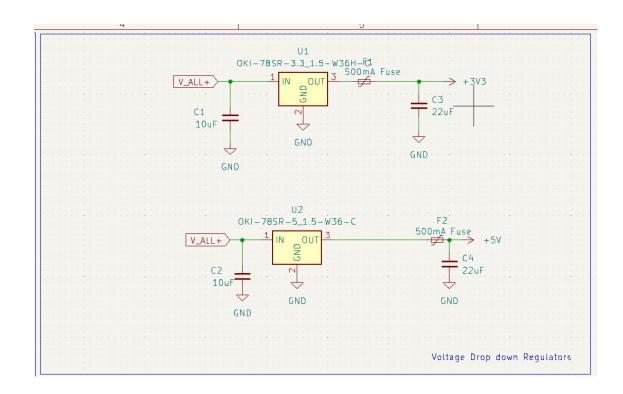

USB C receptacle

USB Voltage drop down:

-LDO linear Regulator

ESP32-S2-SOLO:

assigned GPIO:

-thermocouple: SO, SCK,CS


-LCD I2C: sda,scl

-Fan relay

-Heater relay

-Boot button


-Reset button

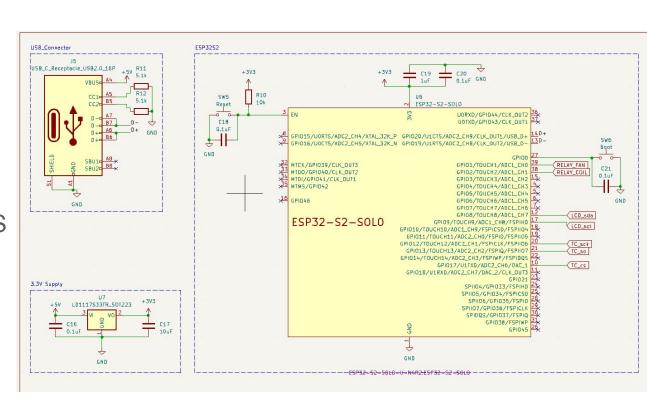
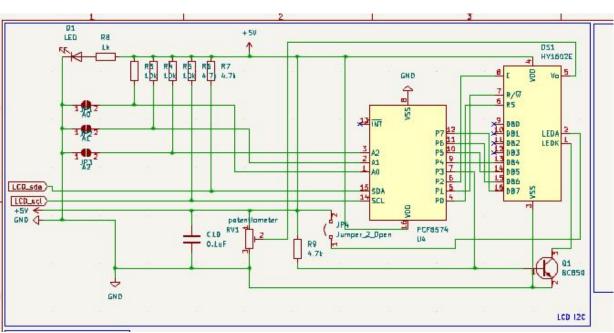
#### LCD I2C:


Generic 20x4 LCD display, replicate I2C board with IO expander






Thermocouple module:

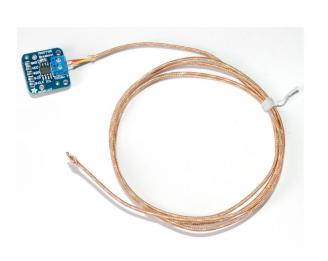
MAX31855 IC, screw terminal connected to k-type thermocouple



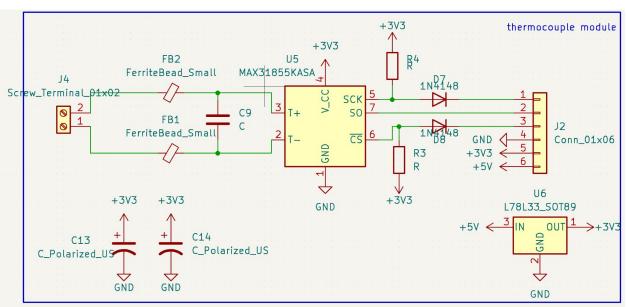


Additional COTS components not included in schematics:

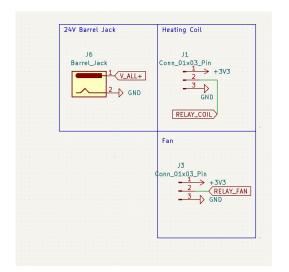- -3V AC relays for Heater and Fan
- -AC/DC converter Barrel Jack → Output 24V 1A, 100 ~ 240 VDC Input


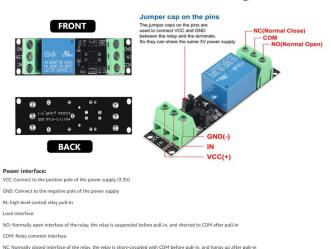
#### 1 Channel 3V/8.3V Power Relay Module






# **Trace Widths**
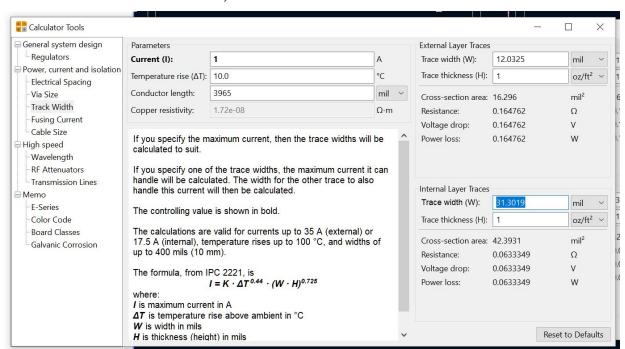
#### 24V 1A DC input:

32 mil trace width, 32 mil via inner diameter, 64 mil via outer diameter:



# **Trace Widths**

## 3.3V and 5V (VUSB) nets, 500mA max:

12.5 mil trace width, 25 mil via inner diameter, 12.5 mil via outer diameter:

+3V3 net

### 5V net

