

# Instructions:

- Copy Title, Overview, BOM, Components, Schematic and Layout templates (the next 5 slides)
- Fill out each slide according to the instructions on the template
- You will be presenting your project to the class, so be ready to talk about the material on your slides. **We are NOT grading you on your presentation skills, but on CONTENT**

# Coffee Bean Roaster

Carlson Jansen  
Andrew Liu  
Mirwais Lodin  
Liam McHugh

# Project Overview and Name ~1 min


- Our project aims for implementing a functional precision temperature control for equipment like a Coffee Bean Roaster, by recycling simple popcorn maker with built in heater, fan, and AC power distribution.
- The project will dive into recreating thermocouple module, AC or DC heat fan dimmer/control board, wall plug AC/DC converter, additional app/GUI control on screen display.
- Major challenges would be precise feedback control of temperature in the chamber, additional serial peripheral interface bus may be required if multiple thermocouple is desired.
- ESP32, K-Type Thermocouple, 16x4 LCD
- Overall circuit designs (filter types, power regulator type, power source, microcontroller used, important sensors, actuators or ICs, data buses used)


## BOM ~30 sec

- Screenshot of BOM, mostly for reference
- **Use multiple slides if necessary**
- Point out expensive parts and the total cost per board

## Schematic ~2 min

- **Add more slides with zoomed-in detail views DO NOT JUST SHOW A ZOOMED OUT PHOTO OF THE ENTIRE SCHEMATIC**
- If you do not know the best way to subdivide the schematic for separate screenshots, we recommend breaking it up by circuit category you fulfill for the project requirements
- Crop whitespace so schematic fills as much as possible
- Make sure image is not low resolution
- Box/label sub-blocks if not already done in the schematic

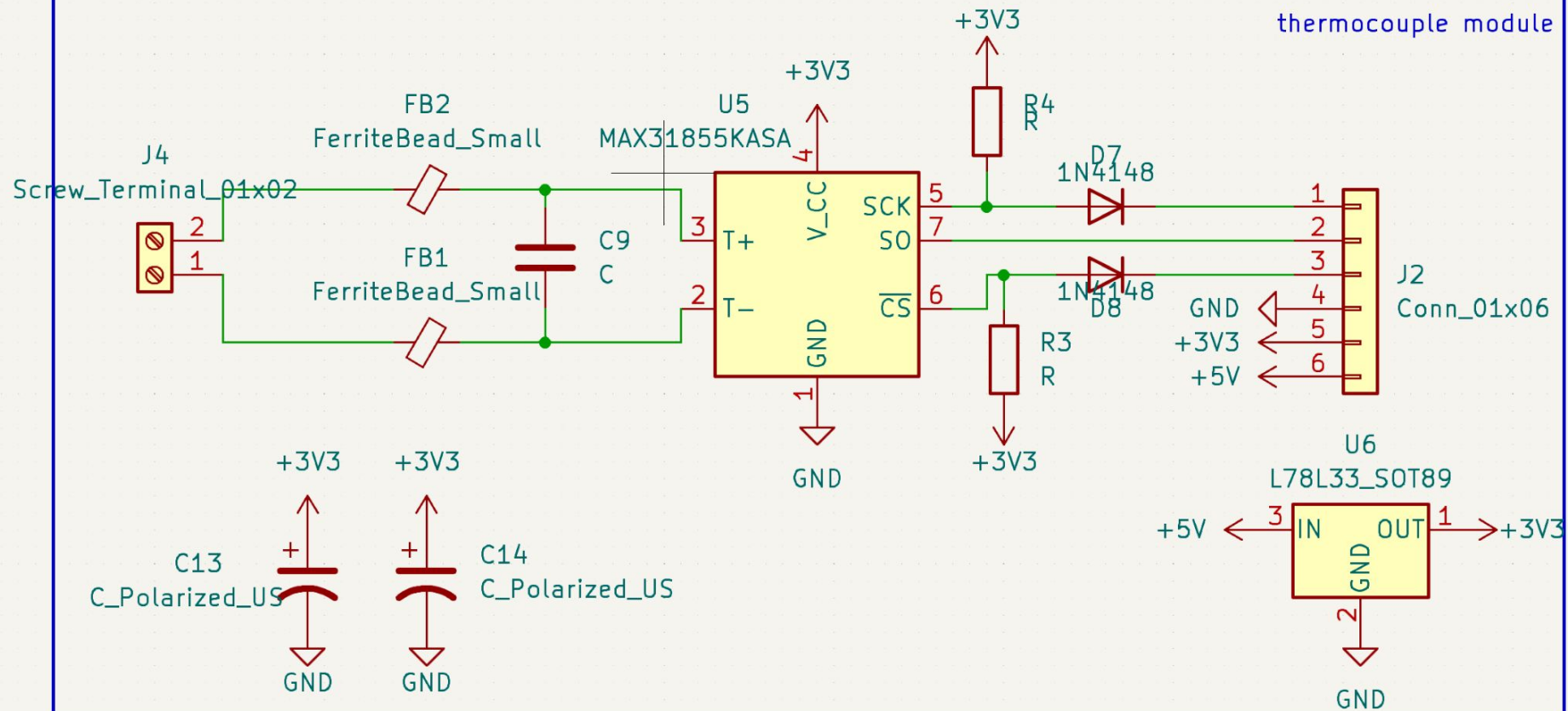

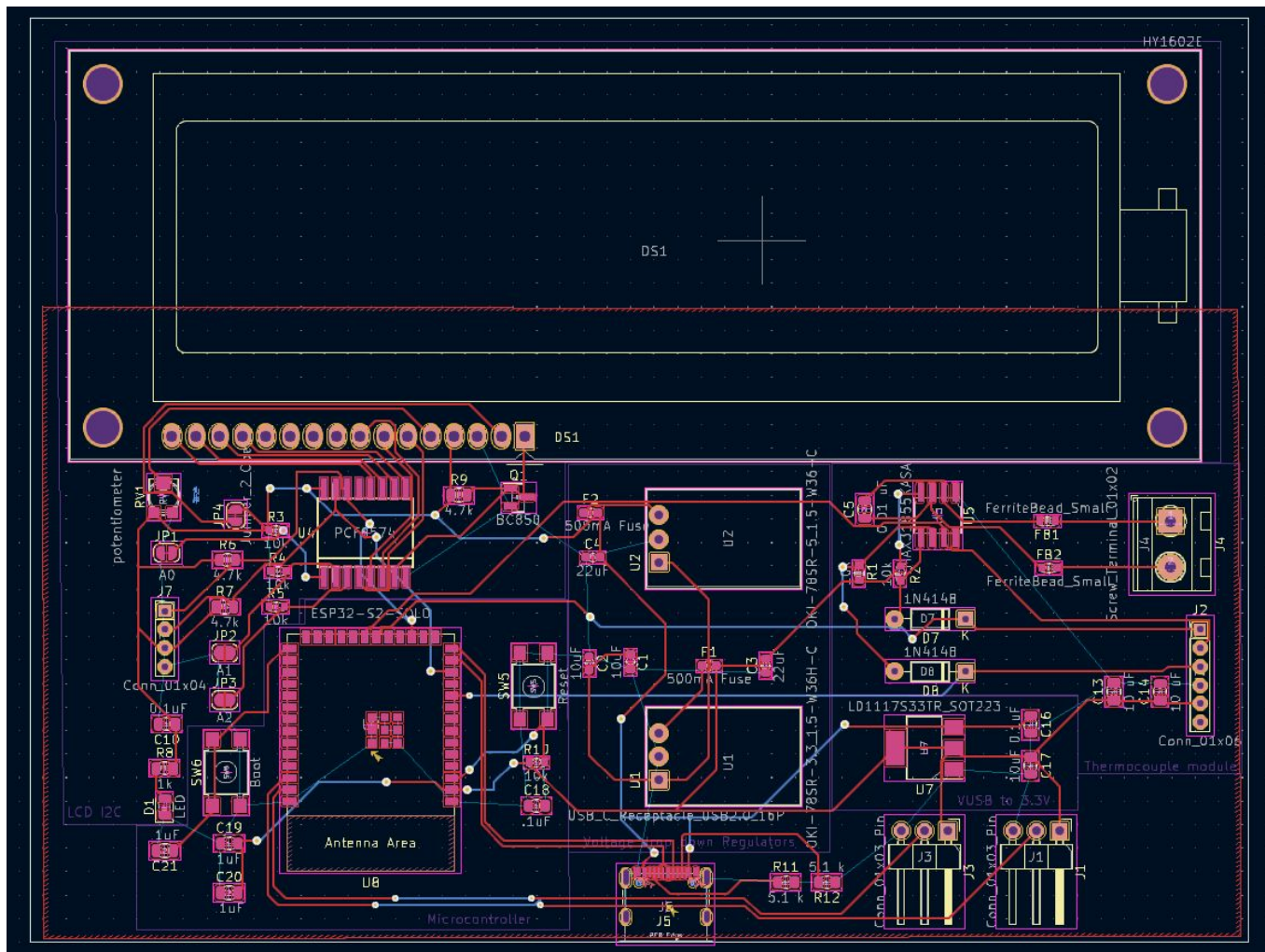


Zoomed In:

Thermocouple MAX 31855 module ----->

VUSB to 3.3V voltage Regulator ----->

Two 1x3 connector Heater & Fan Relays ----->

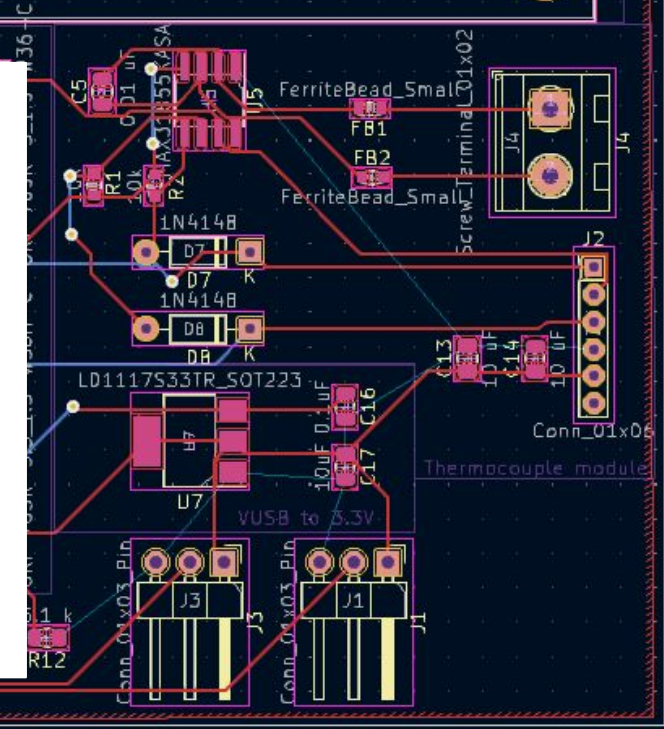







Zoomed In:  
24V DC to 5V Voltage drop down Reg →

24V DC to 3.3V Voltage Regulator →

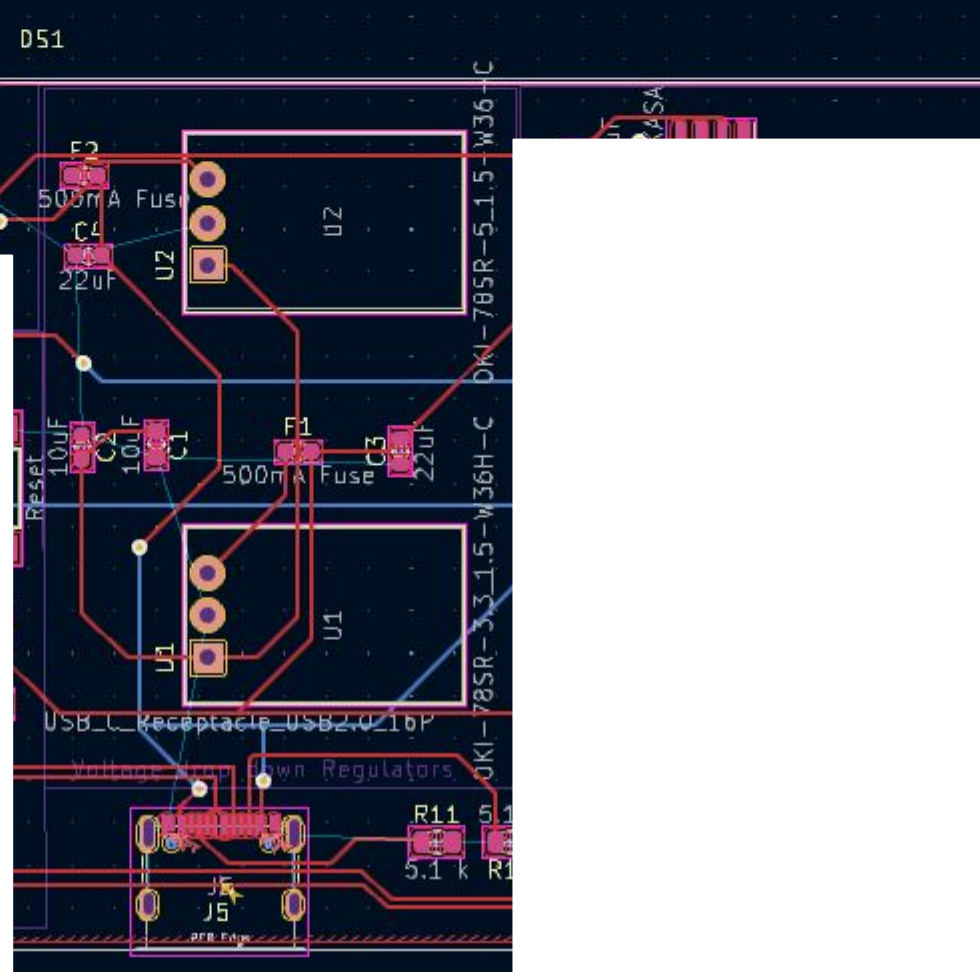

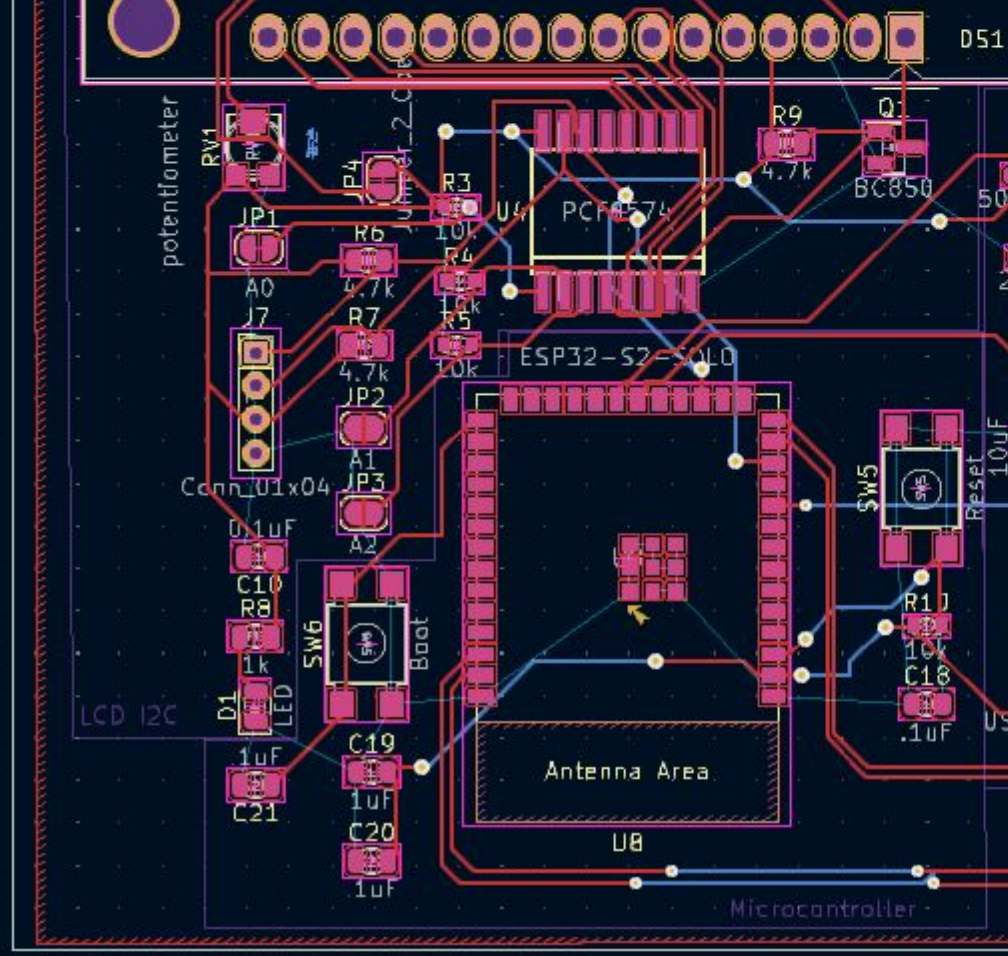

Zoomed In:

← I2C for LCD

← ESP32 S2 SOLO

USBC connector

I  
V

